

Name \_\_\_\_\_  
Date \_\_\_\_\_  
Instructor \_\_\_\_\_

EXPERIMENT  
**6**

# Clamping Circuits

## OBJECTIVE

*To calculate, draw, and measure the output voltage of clampers.*

## EQUIPMENT REQUIRED

### Instruments

Oscilloscope  
DMM

### Components

#### *Resistors*

(1) 100- $\Omega$   
(1) 1-k $\Omega$   
(1) 100-k $\Omega$

#### *Diode*

(1) Silicon

#### *Capacitor*

(1) 1- $\mu$ F

### Supplies

(1) 1.5-V D cell and holder  
Function generator

**EQUIPMENT ISSUED**

Item	Laboratory serial no.
Oscilloscope	
DMM	
Function generator	

**RÉSUMÉ OF THEORY**

Clampers are designed to "clamp" an alternating input signal to a specific level without altering the peak-to-peak characteristics of the waveform. Clampers are easily distinguished from clippers in that they include a capacitive element. A typical clamper will include a capacitor, diode, and resistor with some also having a DC battery. The best approach to the analysis of clampers is to use a step-by-step approach. The first step should be an examination of the network for that part of the input signal that forward biases the diode. Choosing this part of the input signal will save time and probably avoid some unnecessary confusion. With the diode forward biased the voltage across the capacitor and across the output terminals can be determined. For the rest of the analysis it is then assumed that the capacitor will hold on to the charge and voltage level established during this interval of the input signal. The next part of the input signal can then be analyzed to determine the effect of the stored voltage across the capacitor and the open-circuit state of the diode.

The analysis of a clamper can be quickly checked by simply noting whether the peak-to-peak voltage of the output signal is the same as the peak-to-peak voltage of the applied signal. This check is not sufficient to be sure the entire analysis was correct but it is a characteristic of clampers that must be satisfied.

**PROCEDURE****Part 1. Threshold Voltage**

Determine the threshold voltage for the silicon diode using the diode-checking capability of the DMM or a curve tracer. If either approach is unavailable assume  $V_T = 0.7$  V.

$$V_T = \underline{\hspace{2cm}}$$

**Part 2. Clampers (R, C, Diode Combination)**

- a. Construct the network of Fig. 6.1 and record the measured value of  $R$ .

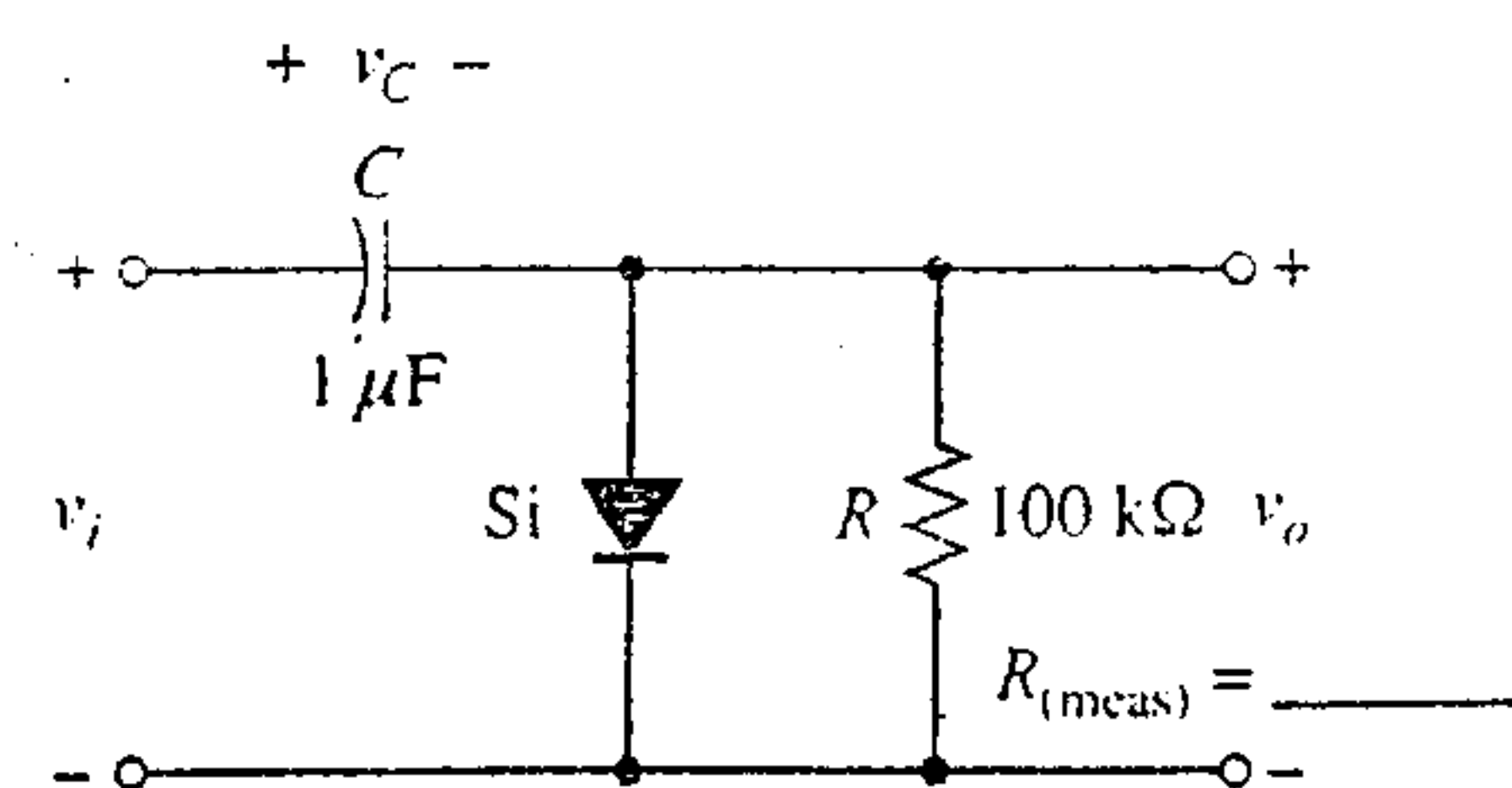
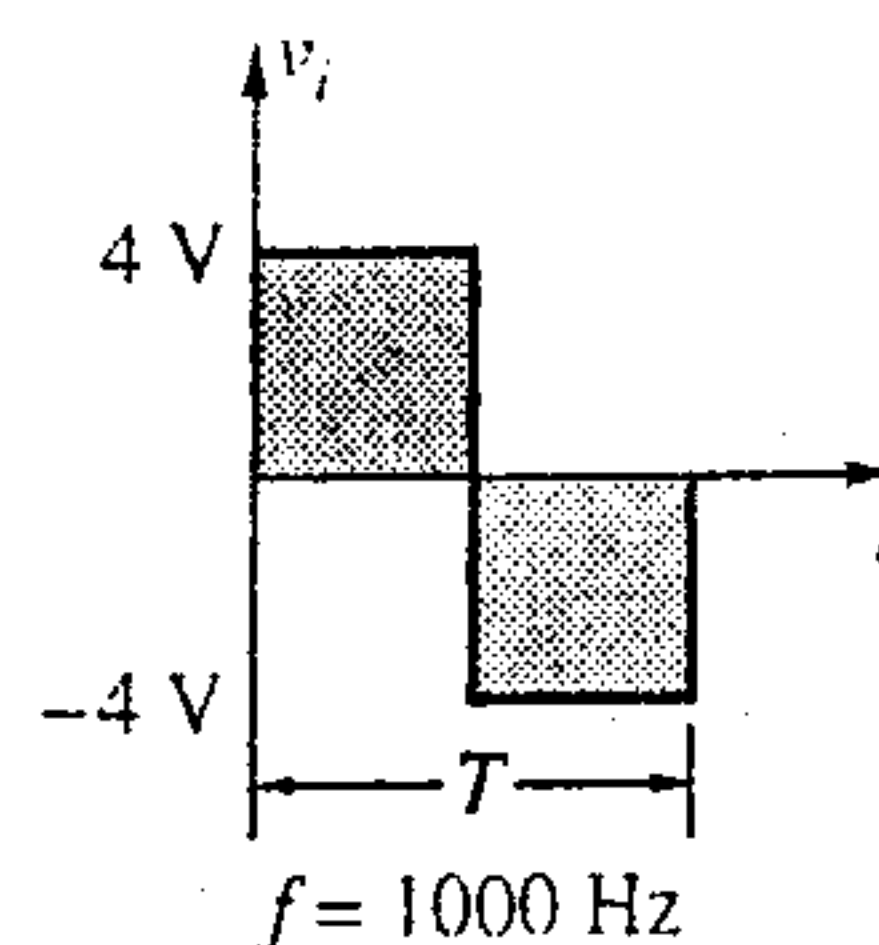


Figure 6-1

- b. Using the value of  $V_T$  from Part 1 calculate  $V_C$  and  $V_o$  for the interval of  $v_i$  that causes the diode to be in the "on" state.

$$V_C \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- c. Using the results of Part 2(b) calculate the level of  $V_o$  after  $v_i$  switches to the other level and turns the diode "off."

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- d. Using the results of Parts 2(b) and 2(c) sketch the expected waveform for  $V_o$  in Fig. 6.2 for one full cycle of  $V_i$ . Use the horizontal center axis as the  $V_o = 0$  V line. Record the chosen vertical and horizontal sensitivities below:

**Sketch of  $V_o$  from calculated results:**

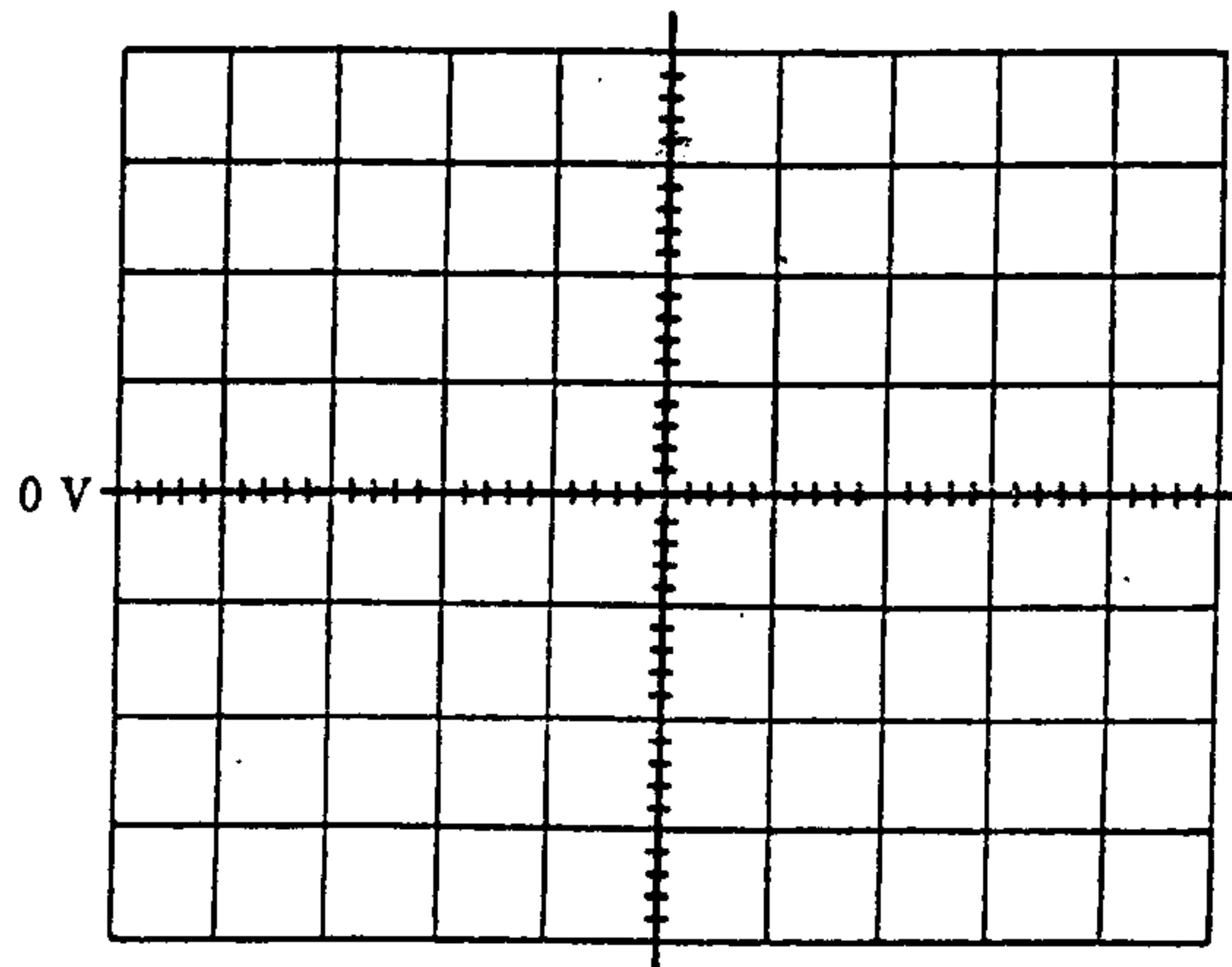


Figure 6-2

$$\text{Vertical sensitivity} = \underline{\hspace{2cm}}$$

$$\text{Horizontal sensitivity} = \underline{\hspace{2cm}}$$

- e. Using the sensitivities of Part 2(b) use the oscilloscope to view the output waveform  $v_o$ . Be sure to preset the  $V_o = 0$  V line on the screen using the GND position of the coupling switch (and the DC position to view the waveform). Record the resulting waveform on Fig. 6.3.

How does the waveform of Fig. 6.3 compare with the expected waveform of Fig. 6.2?

Sketch of  $V_o$  from measured results:

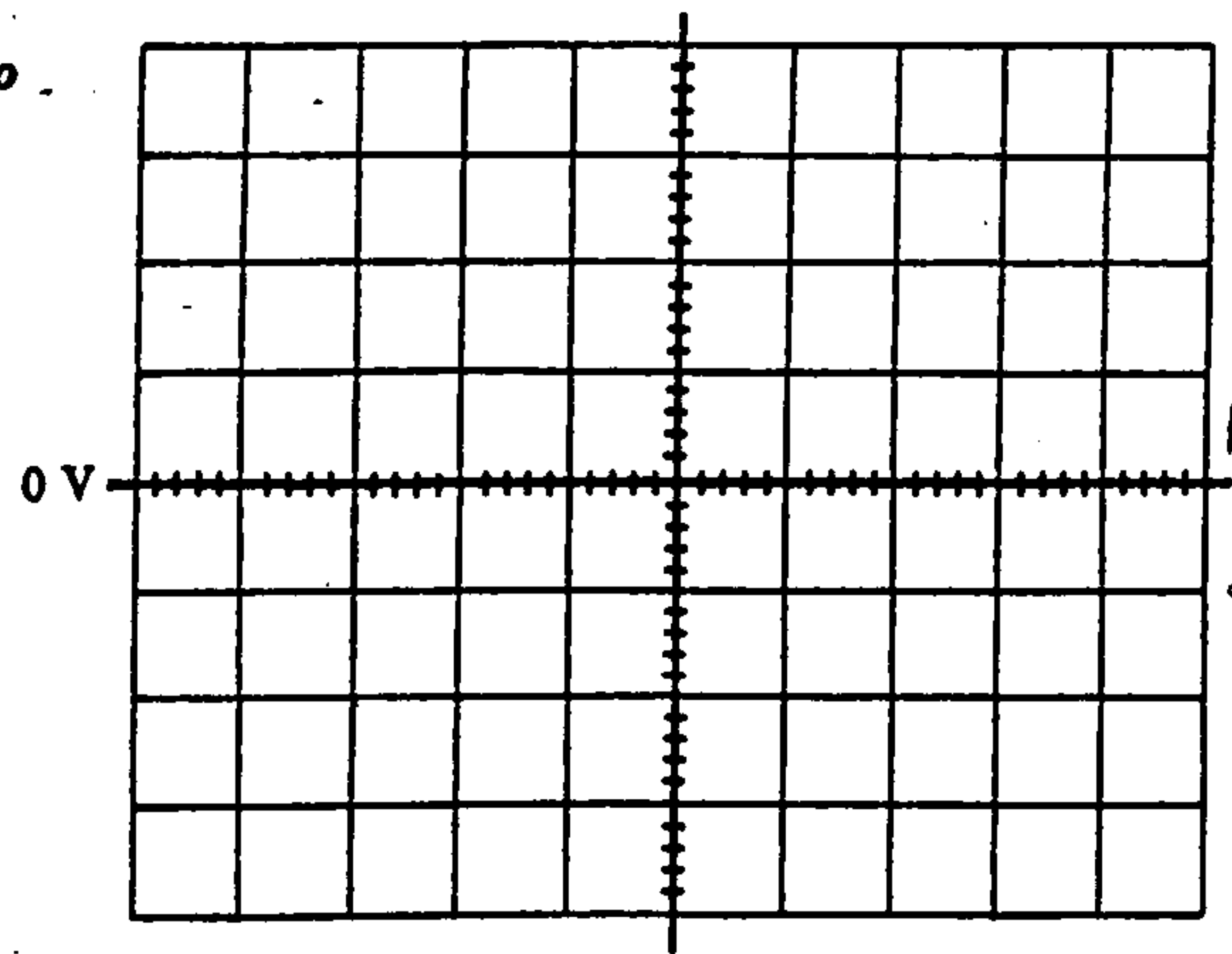


Figure 6-3

- f. Reverse the diode of Fig. 6.1 and using the value of  $V_T$  from Part 1 determine the levels of  $V_C$  and  $V_o$  for the interval of  $v_i$  that causes the diode to be in the "on" state.

$$V_C \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- g. Using the results of Part 2(f) calculate the level of  $V_o$  after  $v_i$  switches to the other level and turns the diode "off."

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- h. Using the results of Parts 2(f) and 2(g) sketch the expected waveform for  $v_o$  on Fig. 6.4. Use the horizontal axis as the  $v_o = 0$  V line. Record the chosen vertical and horizontal sensitivities below:

Sketch of  $V_o$  from calculated response:

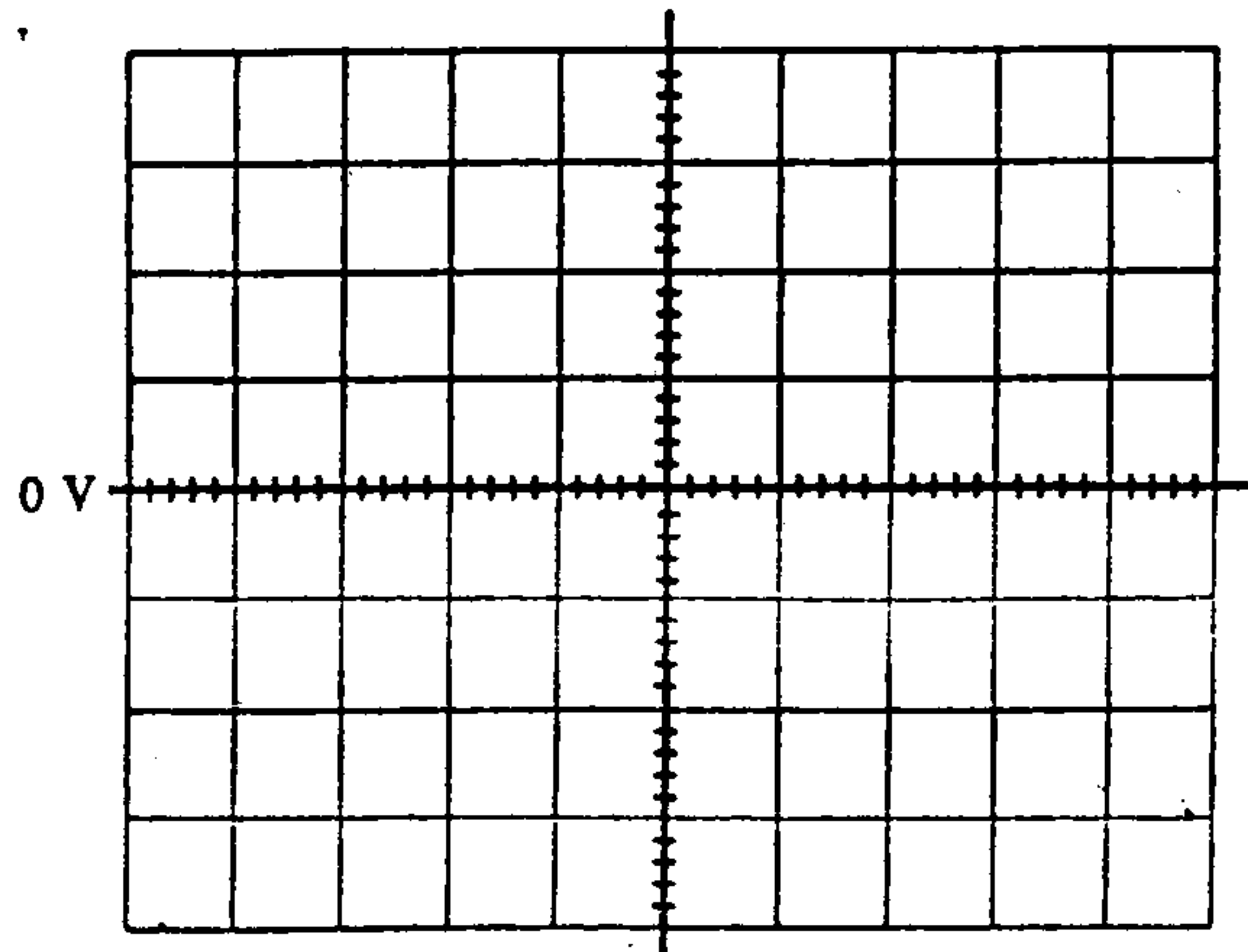


Figure 6-4

$$\text{Vertical sensitivity} = \underline{\hspace{2cm}}$$

$$\text{Horizontal sensitivity} = \underline{\hspace{2cm}}$$

- i. Using the sensitivities of Part 2(h) use the oscilloscope to view the output waveform  $v_o$ . Be sure to preset the  $V_o = 0$  V line on the screen using the GND position of the coupling switch (and the DC position to view the waveform). Record the resulting waveform on Fig. 6.5.

Sketch of  $V_o$   
from  
measured  
results:

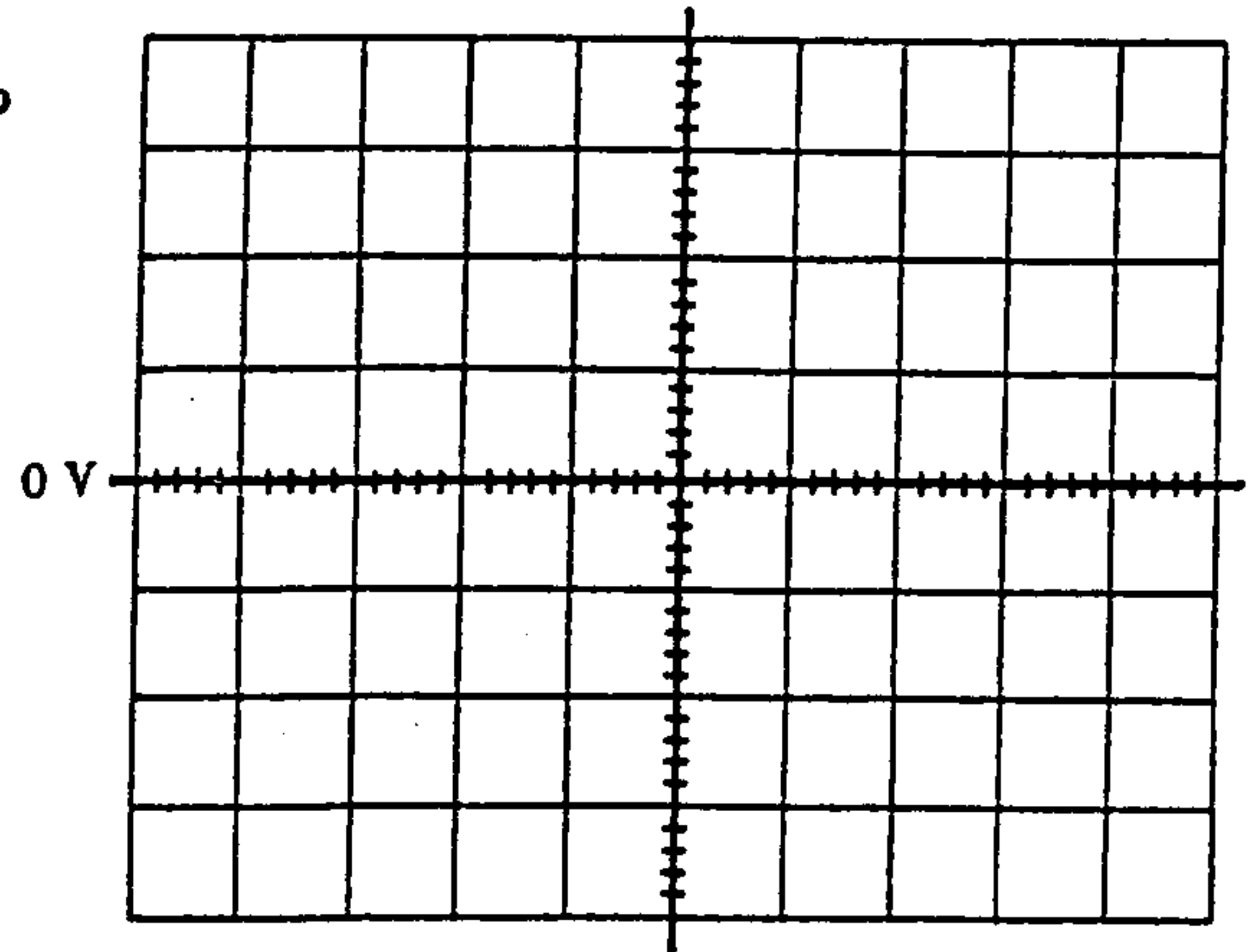


Figure 6-5

How does the waveform of Fig. 6.5 compare with the expected waveform of Fig. 6.4?

### Part 3. Clampers with a DC Battery

- a. Construct the network of Fig. 6.6 and record the measured values of  $R$  and  $E$ .


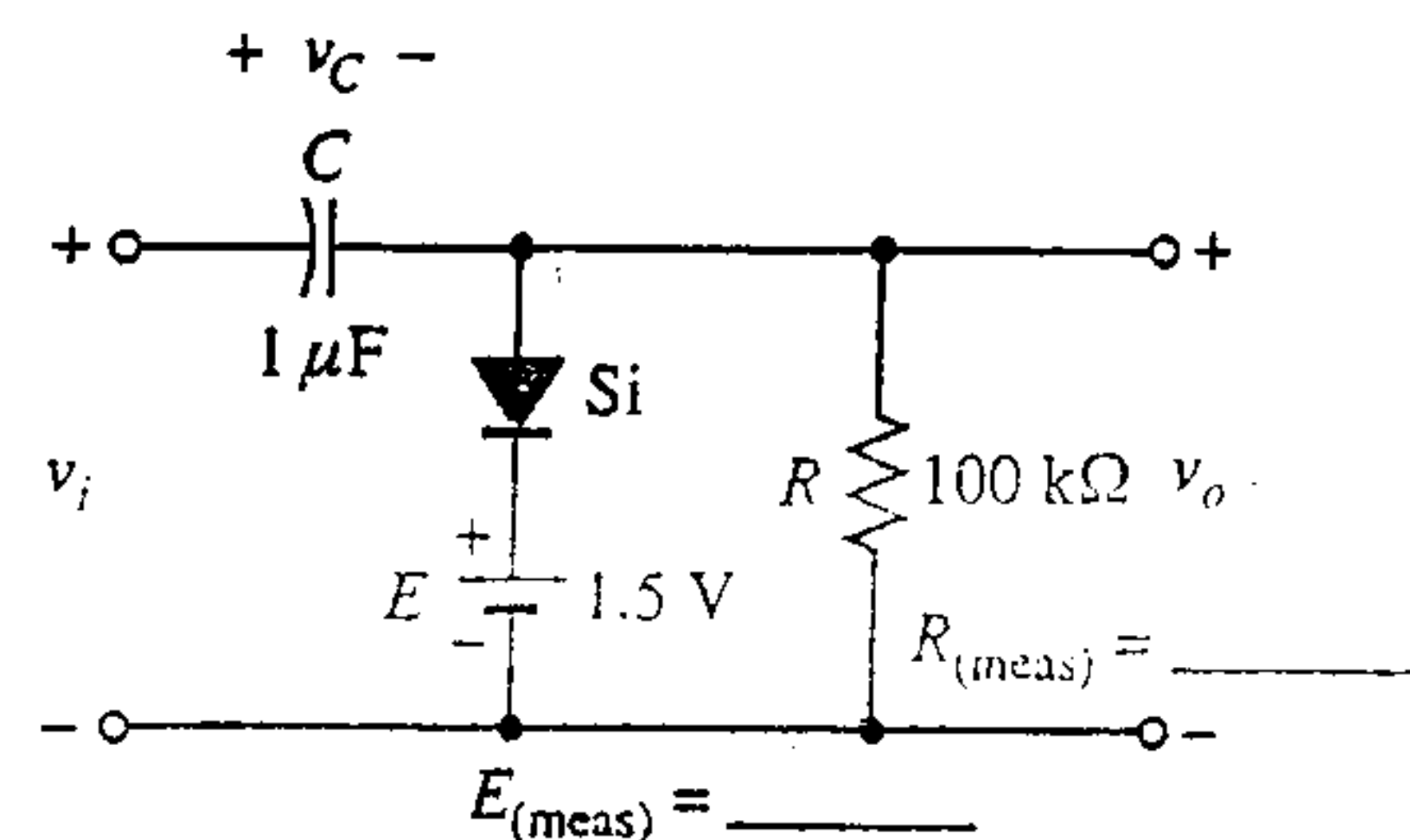


Figure 6-6

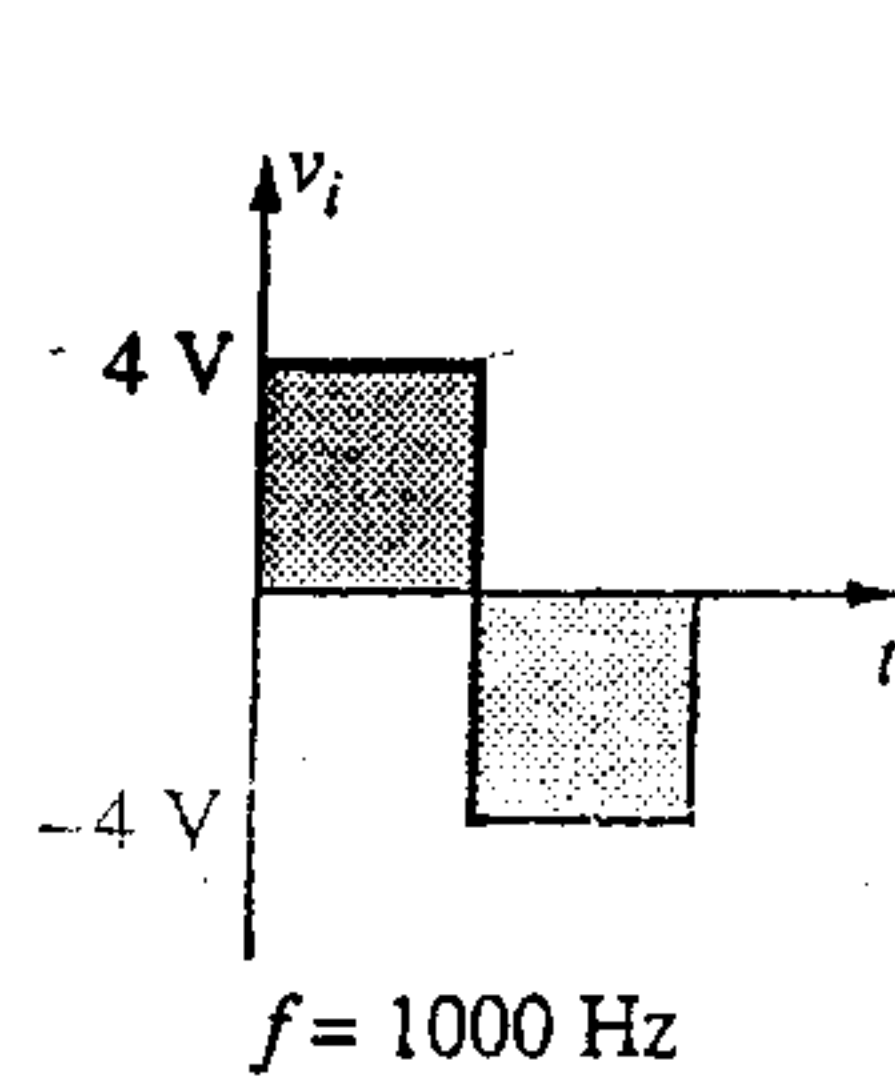

- b. Using the value of  $V_T$  from Part 1 calculate  $V_C$  and  $v_o$  for that interval of  $v_i$  that causes the diode to be in the "on" state.

$$V_C \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- c. Using the results of Part 3(b) calculate the level of  $v_o$  after  $v_i$  switches to the other level and turns the diode "off."

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- d. Using the results of Parts 3(b) and 3(c) sketch the expected waveform for  $v_o$  on Fig. 6.7. Use the horizontal center axis as the  $V_o = 0$  V line. Record the chosen vertical and horizontal sensitivities below:

**Sketch of  $V_o$  from calculated results:**

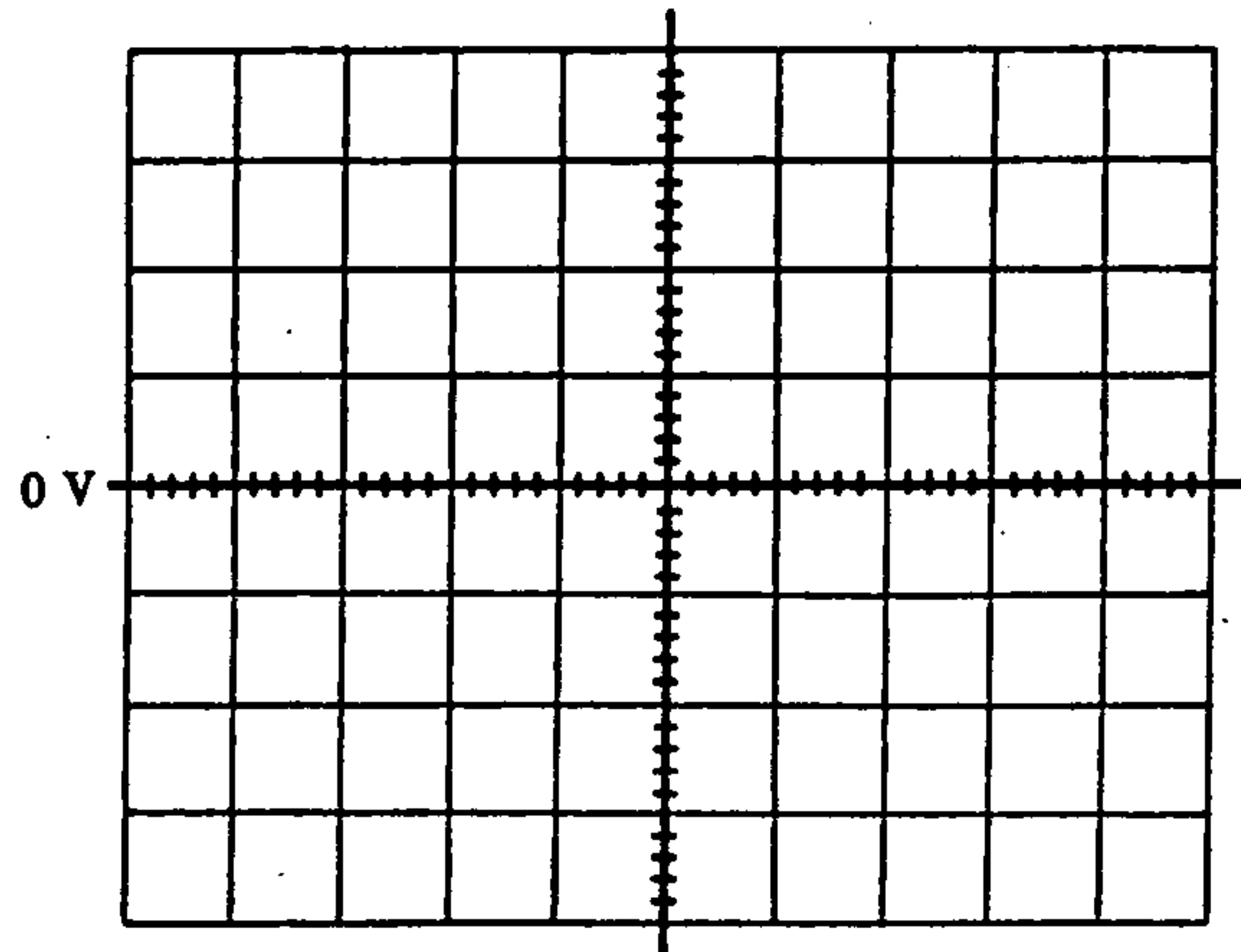


Figure 6-7

$$\text{Vertical sensitivity} = \underline{\hspace{2cm}}$$

$$\text{Horizontal sensitivity} = \underline{\hspace{2cm}}$$

- e. Using the sensitivities of Part 3(d) use the oscilloscope to view the output waveform  $v_o$ . Be sure to preset the  $V_o = 0$  V line on the screen using the GND position of the coupling switch (and the DC position to view the waveform). Record the resulting waveform on Fig. 6.8.

How does the waveform of Fig. 6.8 compare with the expected waveform of Fig. 6.7?

Sketch of  $V_o$   
from  
measured  
results:

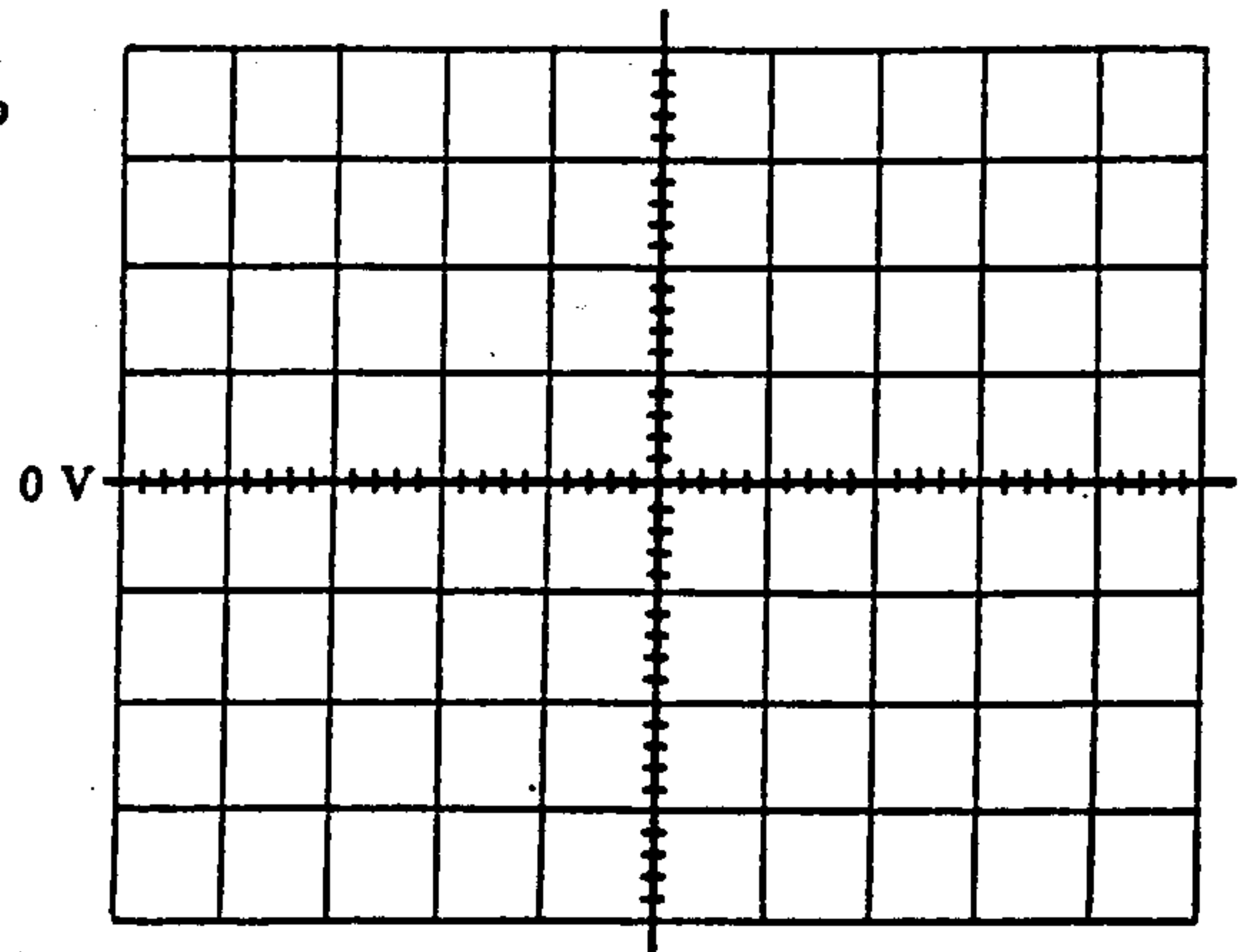


Figure 6-8

- f. Reverse the diode of Fig. 6.6 and using the value of  $V_T$  from Part 1 calculate the levels of  $V_C$  and  $V_o$  for that interval of the input voltage  $v_i$  that causes the diode to be in the "on" state.

$$V_C \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- g. Using the results of Part 3(f) calculate the level of  $V_o$  after  $v_i$  switches to the other level and turns the diode "off."

$$V_o \text{ (calculated)} = \underline{\hspace{2cm}}$$

- h. Using the results of Parts 3(f) and 3(g) sketch the expected waveform for  $v_o$  on Fig. 6.9. Use the horizontal center axis as the  $V_o = 0$  V line. Record the chosen vertical and horizontal sensitivities below:

Sketch of  $V_o$   
from  
calculated  
results:

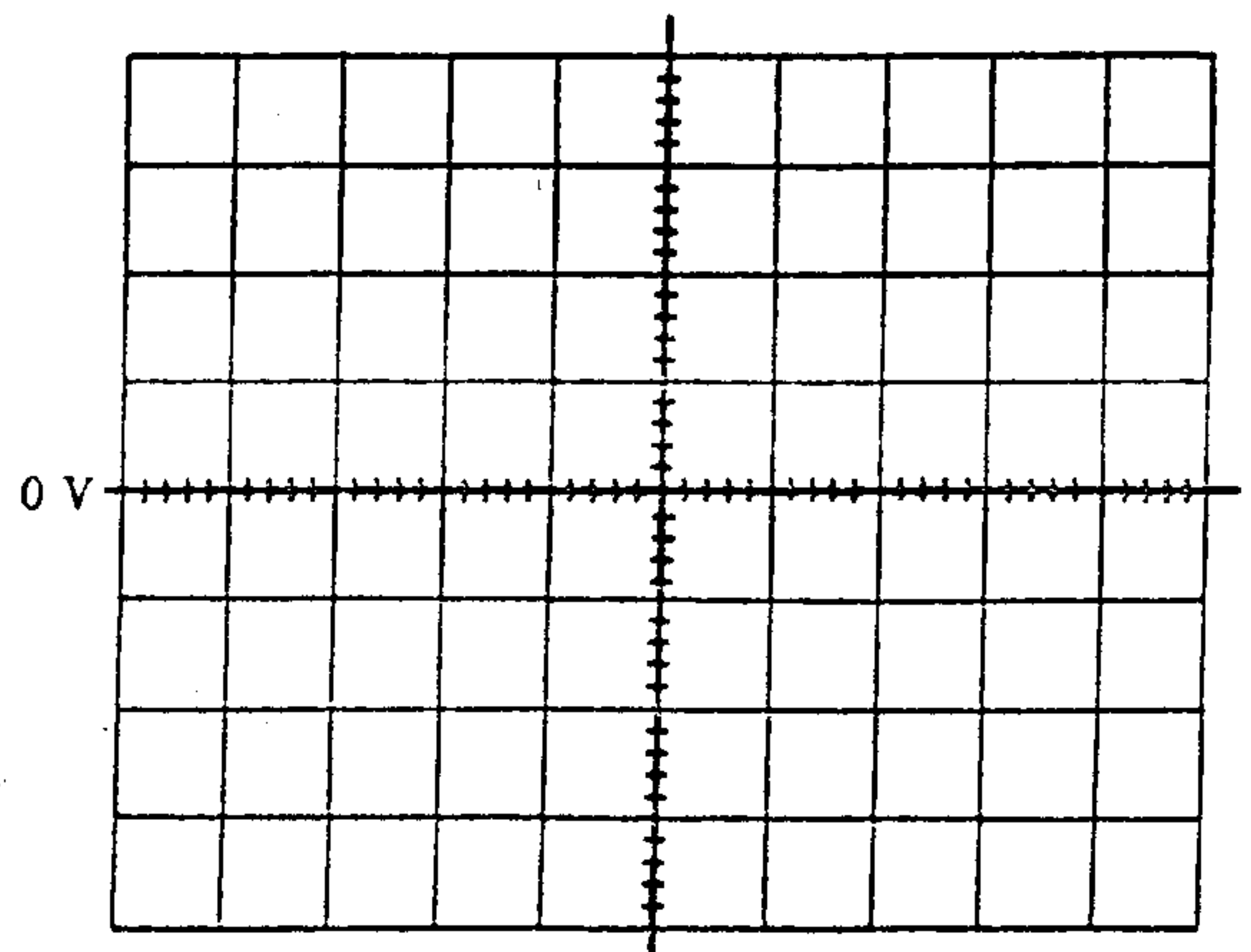


Figure 6-9

Vertical sensitivity = \_\_\_\_\_  
 Horizontal sensitivity = \_\_\_\_\_

- i. Using the sensitivities of Part 3(h) use the oscilloscope to view the output waveform  $v_o$ . Be sure to preset the  $V_o = 0$  V line on the screen using the GND position of the coupling switch (and the DC position to view the waveform). Record the resulting waveform on Fig. 6.10.

**Sketch of  $V_o$   
 from  
 measured  
 results:**

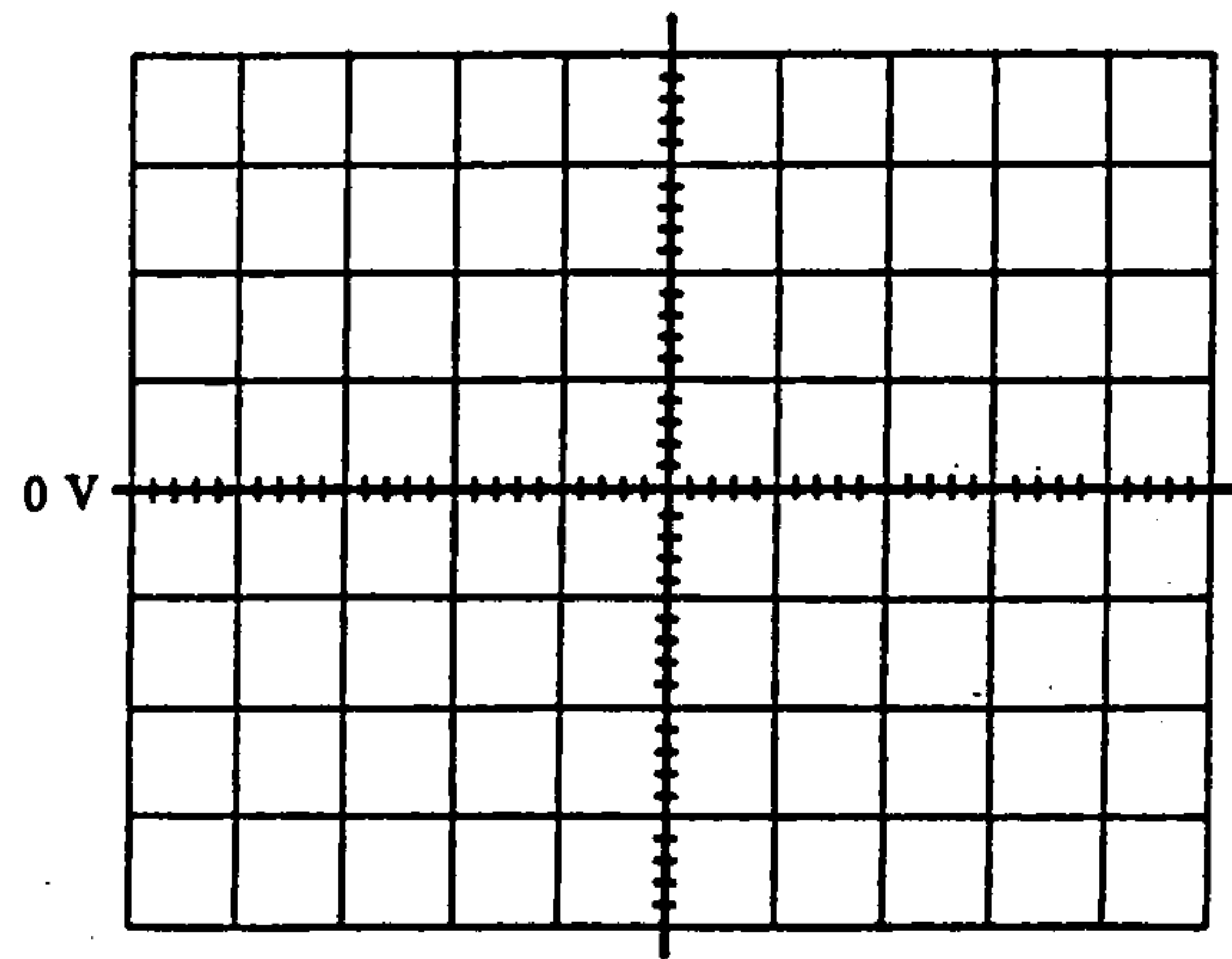


Figure 6-10

How does the waveform of Fig. 6.10 compare with the expected waveform of Fig. 6.9?

**Part 4. Clampers (Sinusoidal Input)**

- a. Reconstruct the network of Fig. 6.1 but change the input signal to an  $8 V_{p-p}$  sinusoidal signal with the same frequency (1000 Hz).
- b. Using the results of Parts 1 and 2 and any other analysis technique at your disposal, sketch the expected output waveform for  $v_o$  on Fig. 6.11. In particular find  $v_o$  when  $v_i$  is its positive and negative peak value and when  $v_i = 0$  V. Record the chosen vertical and horizontal sensitivities below:

**Sketch of  $V_o$   
 from  
 calculated  
 results:**

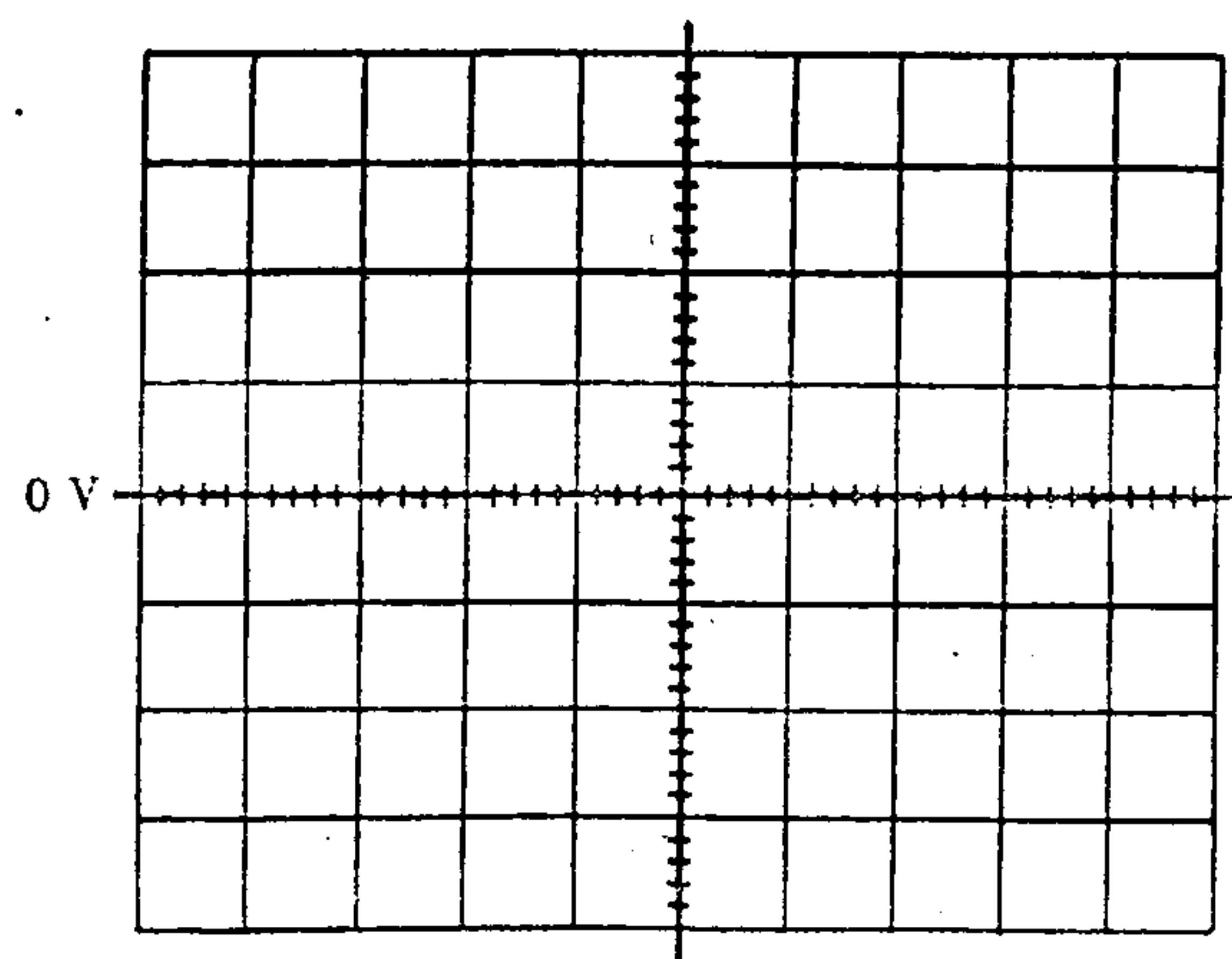


Figure 6-11



$V_o$  (calculated) when  $V_i = +4$  V is \_\_\_\_\_  
 $V_o$  (calculated) when  $V_i = -4$  V is \_\_\_\_\_  
 $V_o$  (calculated) when  $V_i = 0$  V is \_\_\_\_\_  
 Vertical sensitivity = \_\_\_\_\_  
 Horizontal sensitivity = \_\_\_\_\_

- c. Using the sensitivities of Part 4(b) use the oscilloscope to view the output waveform  $v_o$ . Be sure to preset the  $V_o = 0$  V line on the screen using the GND position of the coupling switch (and the DC position to view the waveform). Record the resulting waveform on Fig. 6.12.

**Sketch of  $V_o$   
from  
measured  
results:**

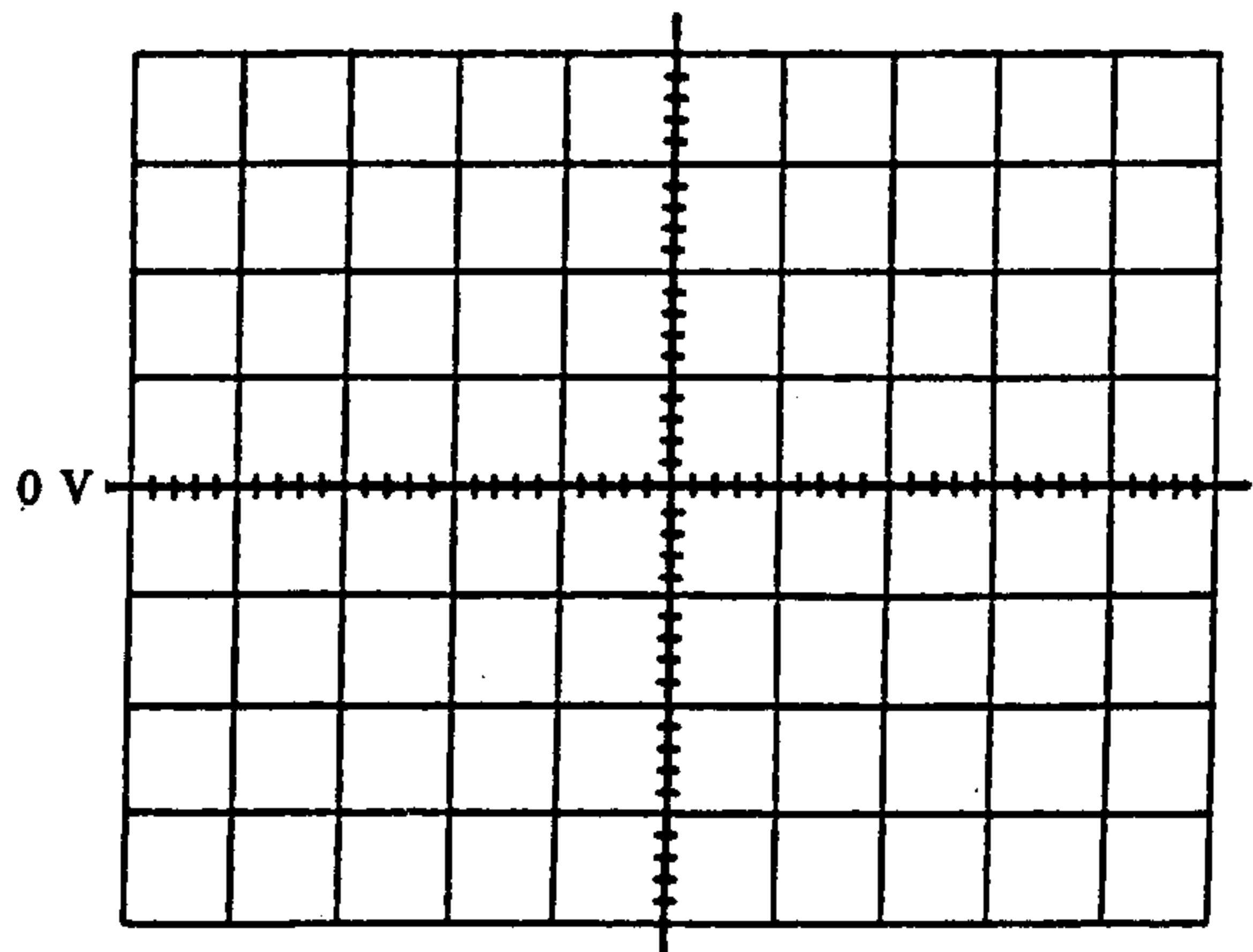


Figure 6-12

How does the waveform of Fig. 6.12 compare with the expected waveform of Fig. 6.11?

**Part 5. Clampers (Effect of  $R$ )**

- a. Determine the time constant ( $\tau = RC$ ) for the network of Fig. 6.1 for that interval of the input signal that causes the diode to assume the "off" state and be approximated by an open circuit.

$\tau$  (calculated) = \_\_\_\_\_

- b. Calculate the period of the applied signal. Determine half the period to correspond with the time interval that the diode is in the "off" state during the first cycle of the applied signal.

$T$  (calculated) = \_\_\_\_\_  
 $T/2$  (calculated) = \_\_\_\_\_

- c. The discharge period of an  $RC$  network is about  $5\tau$ . Calculate the time interval established by  $5\tau$  using the result of Part 5(a) and compare to  $T/2$  calculated in Part 5(b).

$$5\tau \text{ (calculated)} = \underline{\hspace{2cm}}$$

- d. For good clamping action, why is it important for the time interval specified by  $5\tau$  to be much larger than  $T/2$  of the applied signal?

- e. Change  $R$  to  $1 \text{ k}\Omega$  and calculate the new value of  $5\tau$ .

$$5\tau \text{ (calculated)} = \underline{\hspace{2cm}}$$

- f. How does the  $5\tau$  calculated in Part 5(e) compare to  $T/2$  of the applied signal? How would you expect the new value of  $R$  to affect the output waveform  $v_o$ ?

- g. Set the input of Fig. 6.1 with  $R = 1 \text{ k}\Omega$  and record the resulting waveform on Fig. 6.13. Be sure to preset the  $V_o = 0 \text{ V}$  line in the center of the screen using the GND position of the coupling switch and be sure to use the DC position to view the waveform. Insert the chosen vertical and horizontal sensitivities below:

- c. The discharge period of an  $RC$  network is about  $5\tau$ . Calculate the time interval established by  $5\tau$  using the result of Part 5(a) and compare to  $T/2$  calculated in Part 5(b).

$$5\tau \text{ (calculated)} = \underline{\hspace{2cm}}$$

- d. For good clamping action, why is it important for the time interval specified by  $5\tau$  to be much larger than  $T/2$  of the applied signal?

- e. Change  $R$  to  $1 \text{ k}\Omega$  and calculate the new value of  $5\tau$ .

$$5\tau \text{ (calculated)} = \underline{\hspace{2cm}}$$

- f. How does the  $5\tau$  calculated in Part 5(e) compare to  $T/2$  of the applied signal? How would you expect the new value of  $R$  to affect the output waveform  $v_o$ ?

- g. Set the input of Fig. 6.1 with  $R = 1 \text{ k}\Omega$  and record the resulting waveform on Fig. 6.13. Be sure to preset the  $V_o = 0 \text{ V}$  line in the center of the screen using the GND position of the coupling switch and be sure to use the DC position to view the waveform. Insert the chosen vertical and horizontal sensitivities below:

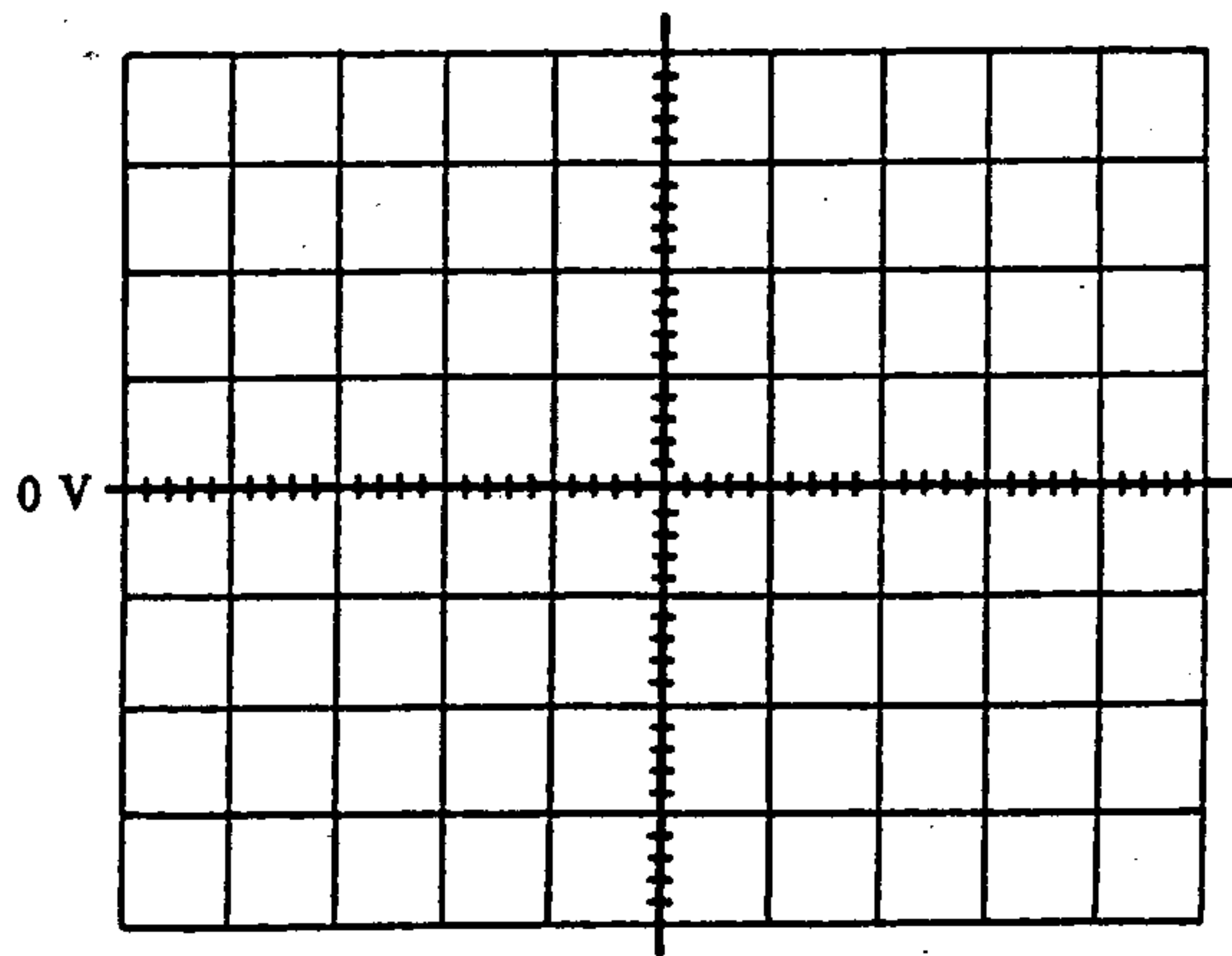


Figure 6-13

Vertical sensitivity = \_\_\_\_\_  
 Horizontal sensitivity = \_\_\_\_\_

**h.** Comment on the resulting waveform of Fig. 6.13. Is the distortion as you expected? Are you surprised by the positive and negative peaks? Why?

**i.** Change  $R$  to  $100 \Omega$  and calculate the new value of  $5\tau$ .

$5\tau$  (calculated) = \_\_\_\_\_

**j.** How does the  $5\tau$  calculated in Part 5(i) compare to  $T/2$  for the applied signal? What effect will the lower value of  $R$  have on the waveform of Fig. 6.13?

**k.** Set the input of Fig. 6.1 with  $R = 100 \Omega$  and record the resulting waveform on Fig. 6.14. Be sure to preset the  $V_o = 0 \text{ V}$  line using the coupling switch and use the DC position to view the waveform  $v_o$ . Insert the chosen vertical and horizontal sensitivities below:

Vertical sensitivity = \_\_\_\_\_  
 Horizontal sensitivity = \_\_\_\_\_





