
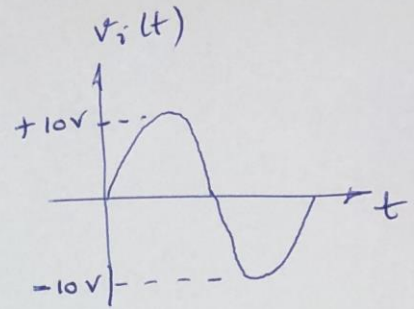


Q.#1.

Final

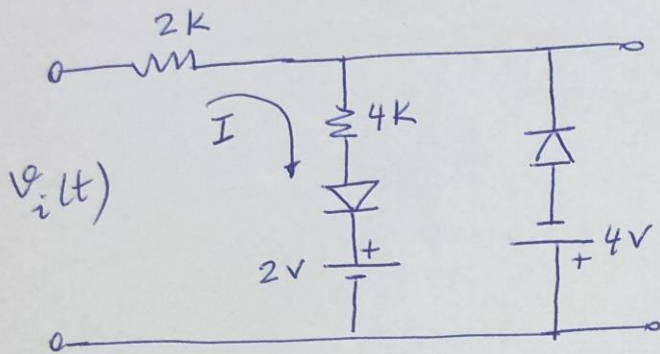

- For the positive half cycle, branch with 4V supply is OPEN circuit.

For $0 < v_i < 2V$ $v_o = v_i$ (6p)

For $v_i \geq 2V$ (7p)

$$-v_i + (2k)I + (4k)I + 2 = 0$$

$$I = \frac{v_i - 2}{6k} \quad ; \quad \text{For } v_i = 10V \Rightarrow I = \frac{(10-2)V}{6k\Omega} = \frac{8}{6} \text{ mA} = 1.33 \text{ mA.}$$


$$v_o = (4k)I + 2 \text{ volts}$$

$$= (4k)(1.33 \text{ mA}) + 2 = 5.32 + 2 = 7.32V.$$


For the negative half cycle; Branch with 2V supply is OPEN circuit.

For $-4V < v_i < 0V$; $v_o = v_i$ (Branch with 4V supply is also OPEN)

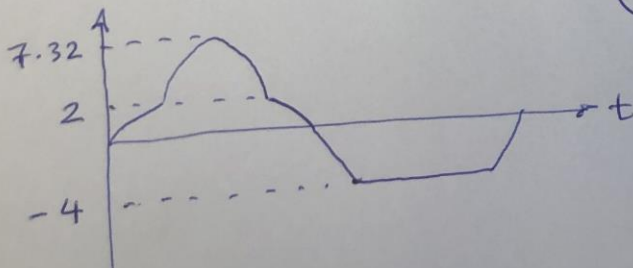For $-10V < v_i \leq -4V \Rightarrow v_o = -4V$ (6p)



Q#2:

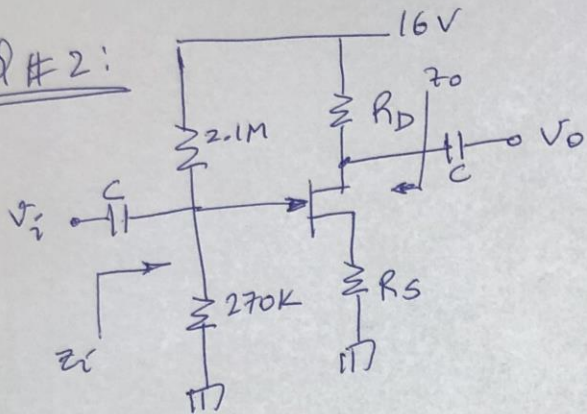

$$I_{DSS} = 5\text{mA} \quad V_p = -4\text{V}$$

$$V_p = 8\text{V} \quad V_s = 3.6\text{V}$$

- (3) $V_G = ? \quad I_{DQ} = ?$ (3)
- (3) $R_D = ? \quad R_S = ?$ (3)
- (3) $I_m = ?$ *SS₀ equiv. model.* (3)
- (3) $A_v = \frac{V_o}{V_i} ? \quad z_i = ? \quad z_o = ?$ (2) (2)


$$V_G = \frac{270\text{K}}{2.1\text{M} + 270\text{K}} \cdot 16\text{V} = (0.114)(16) = \boxed{1.82\text{V}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \quad V_{GS} = V_G - V_s = 1.82 - 3.6 = \boxed{-1.78\text{V}}$$

$$= 5 \left(1 - \frac{-1.78}{-4}\right)^2 = 5(1 - 0.445)^2 = \boxed{1.54\text{mA}}$$

$$R_S = \frac{V_s}{I_{DQ}} = \frac{3.6\text{V}}{1.54\text{mA}} = \boxed{2.33\text{k}\Omega} \quad R_D = \frac{16 - 8}{1.54\text{mA}} = \boxed{5.19\text{k}\Omega}$$

$$I_m = \frac{2I_D}{2V_{GS}} = \frac{2I_{DSS}}{|V_p|} \left(1 - \frac{V_{GS}}{V_p}\right) = \frac{2 \cdot 5\text{mA}}{4\text{V}} \left(1 - \frac{-1.78}{-4}\right) = 2.5\text{m} (0.555) = \boxed{1.38\text{mV}}$$

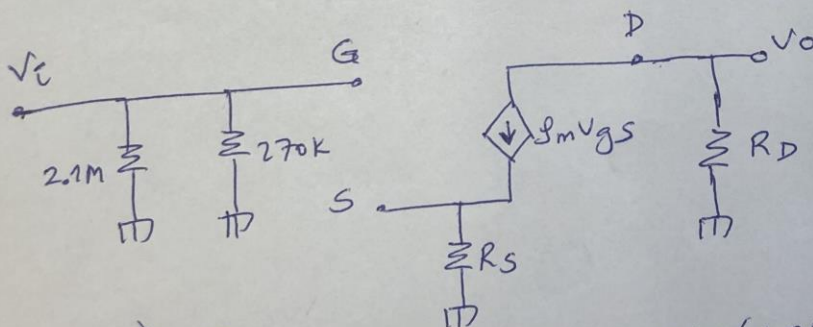

$$V_o = -g_m V_{GS} \cdot R_D$$


$$V_i = V_{GS} + g_m V_{GS} \cdot R_S = V_{GS} (1 + g_m R_S)$$

$$A_v = \frac{-g_m V_{GS} R_D}{V_{GS} (1 + g_m R_S)} = \frac{R_D \cdot g_m}{1 + g_m R_S} = \frac{-5.19\text{K} (1.38 \times 10^{-3})}{1 + (1.38\text{mV})(2.33\text{K}\Omega)} =$$

$$= \frac{-7.16}{1 + 3.22} = \boxed{-1.7} \quad z_i = 270\text{K} \parallel 2.1\text{M} = \boxed{239.2\text{K}\Omega}$$

$$z_o = R_D = \boxed{5.19\text{K}\Omega}$$

Q#3:

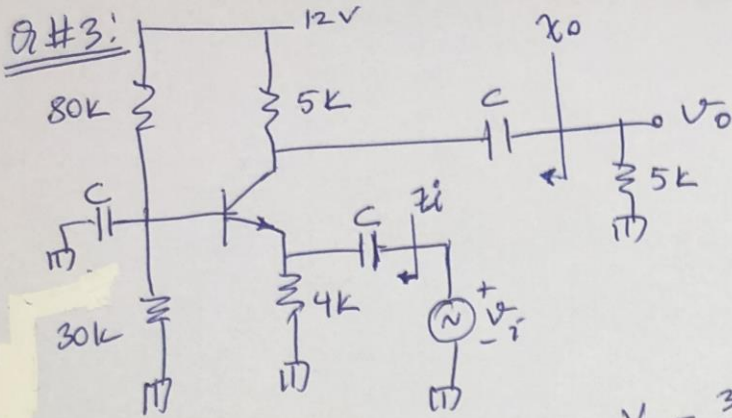

- $\beta = 100$
- (2) $V_{BE} = ?$ (2) $I_{EQ} = ?$ (2) $I_{CQ} = ?$
 - (2) $V_{CEQ} = ?$ s.s.e. r_e model? (3)
 - (2) $r_e = ?$ (3) $A_v = ?$ (3) $A_{v_i} = ?$ (3)
 - (2) $r_i = ?$ (2) $r_o = ?$ (2)
 - What type? (2)

$$V_B = \frac{30k}{30k+80k} \cdot 12V = \boxed{3.27V}$$


Test; $\beta R_E > (10)(30k)$

$(100)(4k) > 300k$ YES ✓

$$V_E = V_B - 0.7 = 3.27 - 0.7 = 2.57V$$

$$I_{EQ} = \frac{V_{EQ}}{R_E} = \frac{2.57V}{4k\Omega} = \boxed{0.64mA}$$
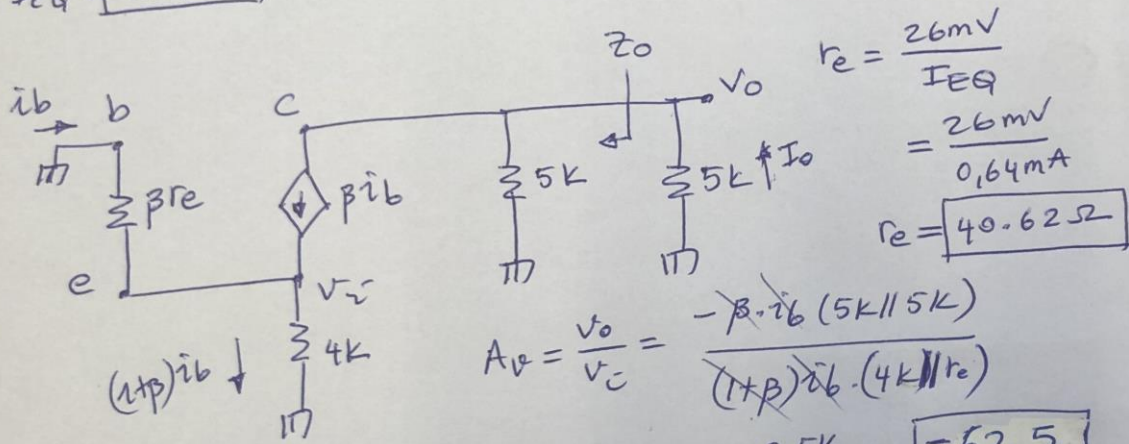
$$I_{CQ} \approx I_{EQ} = \boxed{0.64mA} \quad V_{CEQ} = 12 - (0.64)(5+4) = \boxed{6.24V}$$



$$r_e = \frac{26mV}{I_{EQ}} = \frac{26mV}{0.64mA} = \boxed{40.62\Omega}$$

$$A_v = \frac{v_o}{v_i} = \frac{-\beta \cdot i_b (5k \parallel 5k)}{(1+\beta) i_b (4k \parallel r_e)} = \frac{-2.5k}{40} = \boxed{-62.5}$$


$$I_o = \frac{\beta i_b}{2} \quad I_i \approx -\beta i_b$$

$$A_{v_i} \approx \boxed{0.5}$$

$$r_o = R_C = \boxed{5k\Omega}$$

$$r_{i'} = R_E \parallel r_e = (4k) \parallel (40.62\Omega) = \boxed{40.21\Omega}$$

Q#4:

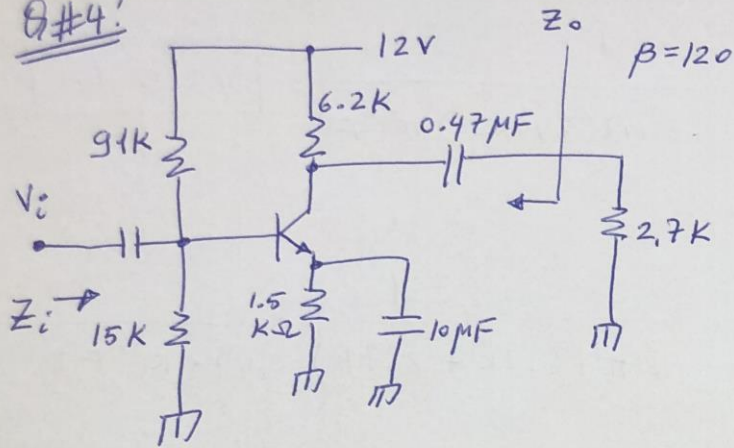

- V_{BQ} (2)
- I_{EQ} (2)
- (2) I_{CQ}
- V_{CEQ} (2)
- (3) sse r_e model
- (2) A_v
- Z_c (2)
- (2) Z_o
- f_{Lc} (2)
- f_{LE} (2)
- f_c (2)

Test ; $\beta R_E > 10 \cdot (R_2)$
 $(120)(1.5k) > 10(15k)$ YES ✓


$$I_{EQ} = \frac{V_{BQ} - 0.7}{1.5k} = \frac{1V}{1.5k}$$

$$= \boxed{0.67mA}$$

$$V_{BQ} = \frac{15k}{15k + 91k} \cdot (12V) = \boxed{1.69V}$$

$$I_{CQ} \approx I_{EQ} = \boxed{0.67mA}$$
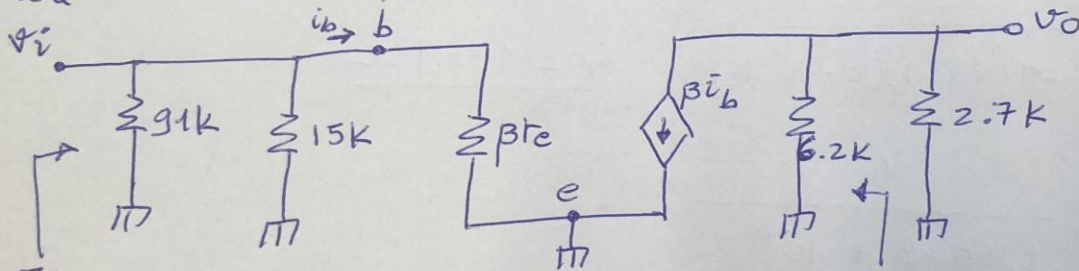
$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) = 12 - 0.67mA(6.2k + 1.5k) = \boxed{6.84V}$$



$$r_e = \frac{26mV}{I_{EQ}} = \frac{26mV}{0.67mA} = \boxed{38.8\Omega}$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b \cdot (6.2k) \parallel (2.7k)}{\beta r_e \cdot i_b}$$

$$= \frac{-1.88k}{38.8\Omega} = \boxed{-48.45}$$

$$V_o = -\beta \cdot i_b \cdot \{(6.2k) \parallel (2.7k)\}$$

$$V_i = \beta \cdot r_e \cdot i_b$$

$$Z_i = (91k) \parallel (15k) \parallel [120(38.8)]$$

$$= \boxed{3.42k\Omega}$$

$$\boxed{Z_o = 6.2k\Omega}$$