

MECE 246 Midterm

(Q1)

$$I_1 + (-I_B) = I_2 \rightarrow I_2 + I_B = I_1 \quad (3)$$

$$\frac{V_B}{R_2} + I_B = \frac{V_{CC} - V_B}{R_1}$$

$$V_B - V_E = 0.7$$

$$I_E = \frac{V_E}{R_E} = \frac{V_E}{10600} \quad I_B = \frac{I_E}{\beta + 1} = \frac{V_E}{10600 \times 100} = \frac{V_B - 0.7}{10600 \times 100}$$

$$\frac{V_B}{6 \times 10^6} + I_B = \frac{12 - V_B}{10^6}$$

$$\frac{V_B}{6 \times 10^6} + \frac{V_B - 0.7}{10600 \times 100} = \frac{12 - V_B}{10^6}$$

$$\frac{V_B}{6} + \frac{V_B - 0.7}{1.06} = \frac{12 - V_B}{1}$$

$$1.96 V_B + 1.6 V_B - 4.2 = 12 \times 6.36 - 6.36 V_B$$

$$6.36 + 1.06 V_B = 12 + 6.36 + 4.2$$

$$(1) V_B = 6 \text{ V} \quad I_B = \frac{V_B - 0.7}{10600 \times 100} = \frac{5.3}{10600 \times 100} = 5 \mu\text{A} \quad I_E = \frac{5.3}{10600} = 500 \mu\text{A} = 0.5 \text{ mA}$$

$$(1) V_E = 5.3 \text{ V}$$

$$(1) I_C = 495 \mu\text{A} = 0.495 \text{ mA}$$

$$= 495 \times 10^{-6} \text{ A}$$


$$V_C = V_{CC} - R_C I_C \quad (4)$$

$$= 12 - \frac{2000}{495} \times 10^6 \times 495 \times 10^{-6}$$

$$V_C = 10 \text{ V}$$

Gides 5

Q2

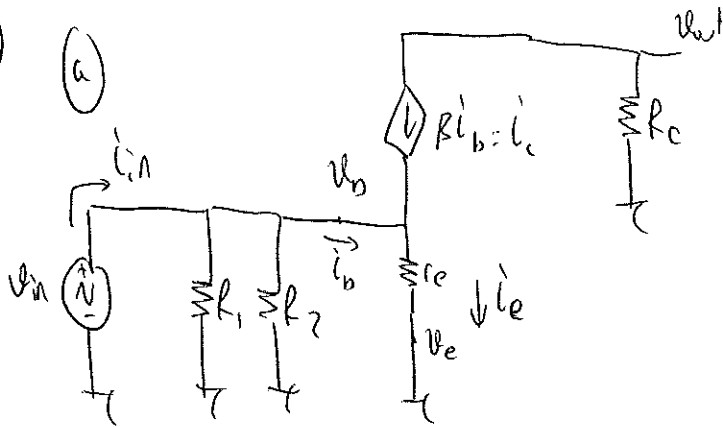

10 puan

her hata için 2 puan gidecek

(b) $i_e = \frac{v_b}{r_e}$ (5) $i_b = \frac{v_b}{(\beta+1)r_e}$ (5)

her hata için 2 puan gidecek

(2) $v_{out} = -\beta i_b R_c$ (15 puan)

(3) $\frac{v_{out}}{v_{in}} = \frac{-\beta i_b R_c}{(\beta+1) r_e i_b} = \frac{-\beta R_c}{\beta+1 r_e}$

(c) $R_{in} = \frac{v_{in}}{i_{in}} \Rightarrow i_{in} = \frac{v_{in}}{R_1} + \frac{v_{in}}{R_2} + \frac{v_{in}}{r_e(\beta+1)}$ (10)

$i_{in} = i_{R1} + i_{R2} + i_b$ (3)



15 puan

$\frac{v_{in}}{i_{in}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_e(\beta+1)}} = [R_1 // R_2 // r_e(\beta+1)]$ (2)

her hata için 2 puan gidecek



Q3

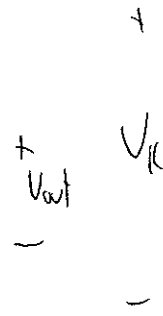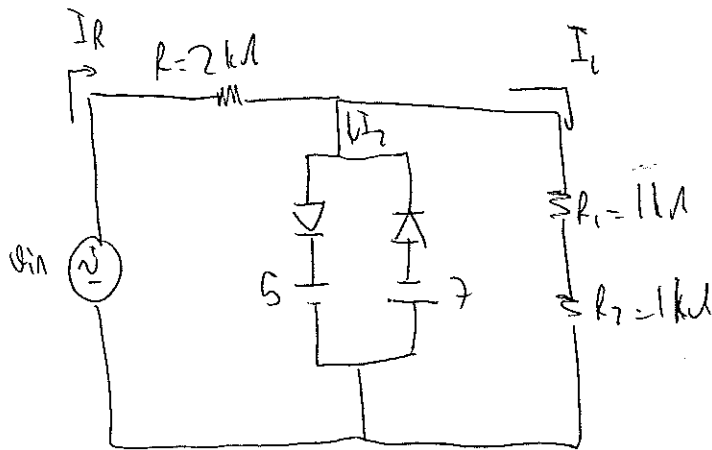

$$V_{out} = \frac{V_k \times 1000}{2000}$$


$$V_{out} = \frac{V_k}{2}$$

When $V_k = 5$ Volt and $I_7 = 0$

$$\frac{V_{in} - V_k}{R} = \frac{V_k}{R_1 R_2} \quad \frac{V_{in} - 5}{2000} = \frac{5}{2000} \Rightarrow V_{in} = 10 \text{ Volt}$$

When $V_k = -7$ Volt and $I_7 = 0$
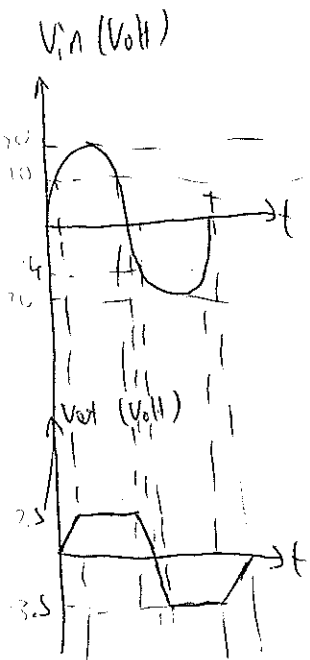
$$\frac{V_{in} - V_k}{R} = \frac{V_k}{R_1 R_2} \quad \frac{V_{in} - (-7)}{2000} = \frac{-7}{2000} \Rightarrow V_{in} = -14 \text{ Volt}$$



if $-14 < V_{in} < 10$ $I_p = I_L = \frac{V_{in}}{R_1 R_2} = \frac{V_{in}}{4000}$

$$V_{out} = I_L R_1 = \frac{V_{in}}{4000} \times 1000 = \frac{V_{in}}{4}$$

if $10 < V_{in}$, $V_k = 5$ Volt, $V_{out} = 2.5$ Volt

if $V_{in} < -14$, $V_k = -7$ Volt, $V_{out} = -3.5$ Volt

circian (10)

limit bo 8 pua

degakar (12)