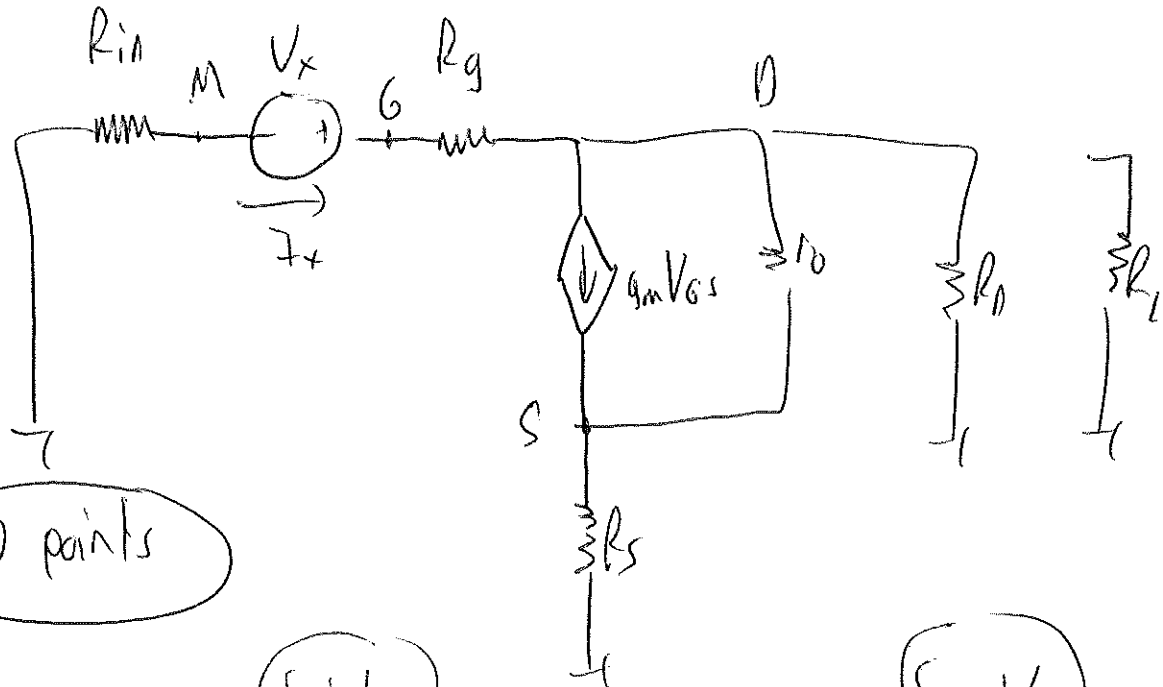


Q1

$R_o = 500$ $R_{in} = 500$



10 points

5 points

5 points

$$\frac{G-D}{R_G} = g_m V_{GS} + \frac{V_D - V_S}{r_o} + \frac{V_D}{R_D}$$

$$g_m V_{GS} + \frac{D-S}{r_o} = \frac{S}{R_S}$$

$$\frac{G-D}{500} = \frac{1}{1000} (G-S) + \frac{D-S}{1000} + \frac{V_D}{1000}$$

$$\frac{1}{1000} (G-S) + \frac{D-S}{1000} = \frac{S}{1000}$$

$$2G - 2D = G - S + D - S + D$$

$$G - S + D - S = S$$

$$2G = 4D - 2S + 6$$

$$G + D = 3S$$

$$G = 4D - 2S$$

$G = 40 - 2S$ $G = 35 - D$

$40 - 2S = 35 - D$

$5D = 5S$

$D = S$; $G = 25 = 2D$

4 puan

$G - M = V_x$

$I_x = g_m V_{GS} + \frac{D-S}{r_o} + \frac{D}{R_D}$

$M = -R_{in} I_x$

$I_x = \frac{1}{1000} (G-S) + \frac{D-S}{1000} + \frac{D}{1000}$

prosedür
9 puan

$G = M + V_x$

$I_x = \frac{1}{1000} [G + 2D - 2S] = \frac{G}{1000}$

$I_x = \frac{M + V_x}{1000}$

$1000 I_x = M + V_x$

$1000 I_x = (-R_{in} I_x) + V_x$

$(1000 + R_{in}) I_x = V_x$

$R_{eq} = \frac{V_x}{I_x} = 1000 + R_{in} = 1500 \Omega$

sonuç 2 puan

$\omega_{cut-off} = \frac{1}{C_g R_{eq}}$

$\omega_{cut-off} = \frac{1}{10^{-6} f + 1500 \Omega}$

$\omega_{cut-off} = \frac{10^6}{1500} = \frac{10^3}{1.5} \frac{rad}{sec}$

Q2

$$(a) R_{in} = \frac{V_{in}}{I_{in}}$$

$$(I_b + \beta I_b) r_e = V_b$$

$$I_b (1 + \beta) r_e = V_b$$

$$I_{in} = \frac{V_b}{R_x} + I_b$$

$$I_{in} = \frac{V_b}{R_x} + \frac{V_b}{(1 + \beta) r_e}$$

$$I_{in} = \frac{V_{in} - V_b}{R_a}$$

$$I_{in} = \frac{V_{in} - V_b}{R_a} = \frac{V_b}{R_x} + \frac{V_b}{(1 + \beta) r_e}$$

5 mark

$$V_{in} = R_a I_{in} + V_b$$

$$\frac{V_{in}}{I_{in}} = R_a + \frac{V_b}{I_{in}} = R_a + \left(R_x // (1 + \beta) r_e \right)$$

1 mark

$$= R_a + \frac{R_x r_e (1 + \beta)}{R_x + r_e (1 + \beta)}$$



1 mark

Q2

(b)

Circuit

V_{in} shorted

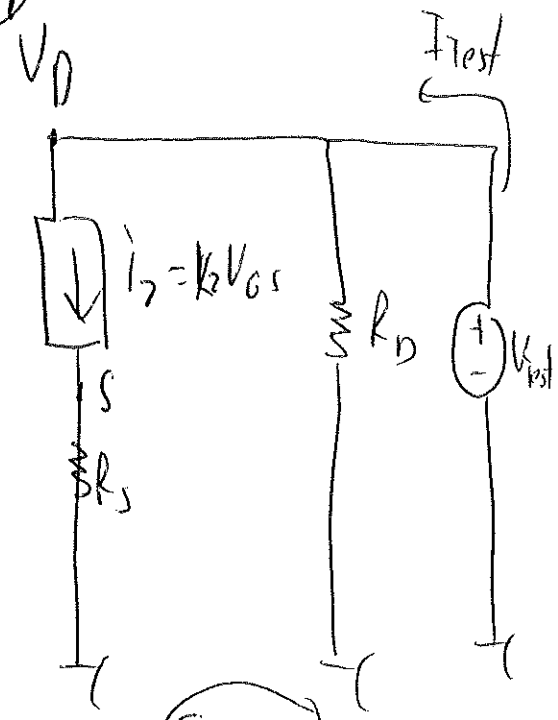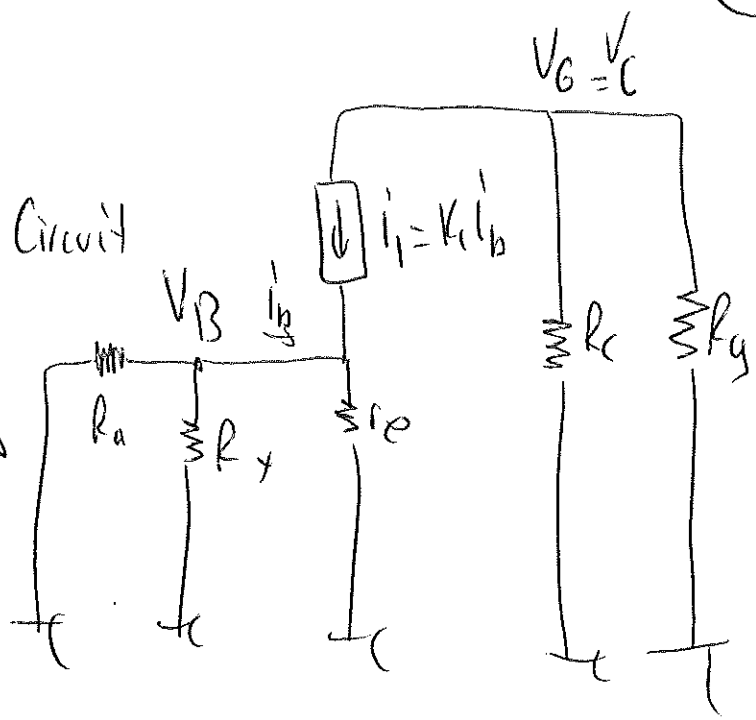

$$V_b = (i_b + k_1 i_b) r_e = (k_1 + 1) i_b r_e$$

5 puan
doire

$$\frac{V_b}{R_a} + \frac{V_b}{R_x} + i_b = 0 \quad V_b \left[\frac{1}{R_a} + \frac{1}{R_x} + \frac{1}{(k_1 + 1) r_e} \right] = 0 \quad V_b = 0$$

5 puan

if $V_b = 0$ $i_b = 0$ $i_1 = k_1 i_b = 0$ $V_G = V_C = 0$

2 puan

$$I_{Test} = \frac{V_{test}}{R_D} + i_2 = \frac{V_{test}}{R_D} + k_2 (V_{os})$$

2 puan

$$I_{Test} = \frac{V_{test}}{R_D} + k_2 (V_G - V_s)$$

$$V_s = I_2 R_s$$

$$V_s = k_2 V_{os} R_s$$

$$V_s = k_2 [0 - V_s] R_s$$

$$V_s [1 + k_2 R_s] = 0 \quad V_s = 0$$

$$I_{Test} = \frac{V_{test}}{R_D} + \left(-\frac{V_s}{1} k_2 \right)$$

2 puan

$$I_{test} = \frac{V_{test}}{R_D} + K_2 V_{os} \Rightarrow \frac{V_{test}}{R_D} + K_1 (0 - 0)$$

$$I_{test} = \frac{V_{test}}{R_D}$$

$$R_{out} = \frac{V_{test}}{I_{test}} = R_D$$

2 pua

Q3

$$\frac{V_D - V_0}{R_1} = \frac{V_0}{R_2} \quad (10 \text{ puan})$$

$$\frac{10 - V_0}{5 \times 10^7} = \frac{V_0}{5 \times 10^7} \quad V_0 = 5 \text{ Volt} \quad (5 \text{ puan})$$

$$I_D = 0.5 (V_{DS} - V_T)^2 \quad R_S = 1000 \Omega$$

$$I_D = 0.5 (5 - V_{DS} - 1)^2 = \frac{V_{DS}}{R_S} \quad (3 \text{ puan})$$

$$R_D = 1000 \Omega$$

$$0.5 (4 - V_{DS})^2 = \frac{V_{DS}}{1000}$$

$$(0.5) (4 - V_{DS})^2 = V_{DS}$$

$$(4 - V_{DS})^2 = 2V_{DS}$$

$$16 - 8V_{DS} + V_{DS}^2 = 2V_{DS}$$

$$V_{DS}^2 - 10V_{DS} + 16 = 0$$

$$(V_{DS} - 2)(V_{DS} - 8)$$

~~$$(V_{DS} - 2)(V_{DS} - 8) = 0$$~~

~~$$V_{DS} - 10V_{DS} + 16 = 0$$~~

$$V_{DS} = 2 \text{ (valid)} \rightarrow (3 \text{ puan})$$

$$V_{DS} = 8 \text{ (not valid)}$$

$$I_D = \frac{V_{DS}}{R_S} = \frac{2}{1000} = 2 \text{ mA}$$

4 puan

5 puan

$$\frac{10 - V_D}{R_D} = I_D = 2$$

$$V_D = 8 \text{ Volt}$$

$$\frac{10 - V_D}{1000} = 2 \text{ mA}$$