

* when $R_L = 0$ $I_Z = 0$ $I_R = I_L = \frac{V_{in}}{R + R_L} = \frac{V_{in}}{10000} = \frac{15}{1000} = 15 \text{ mA}$
 $V_L = R_L I_L = 0 \text{ Volt}$

* when $0 < R_L < R_{critical}$ $I_Z = 0$ $I_R = I_L$
 - to find $R_{critical}$, at $R_L = R_{critical}$ $V_L = 10 \text{ Volt}$ and $I_R = I_L$

$I_R = I_L \Rightarrow \frac{V_{in} - V_{critical}}{R} = \frac{V_{critical}}{R_{critical}}$
 $10 = V_{critical}$ (3)

$I_L = 5 \text{ mA} = \frac{15 - 10}{1000} = \frac{10}{R_{critical}}$

$R_{critical} = \frac{10000}{5} = 2000 \Omega$ (4)



hence

when $0 < R_L < R_{critical} = 2000$ (3)


$I_R = I_L = \frac{V_{in}}{R + R_L} = \frac{15}{1000 + R_L}$
 $V_L = R_L I_L = \frac{15 R_L}{1000 + R_L}$ (4)

* when $R_L > R_{critical} = 2000 \Omega$

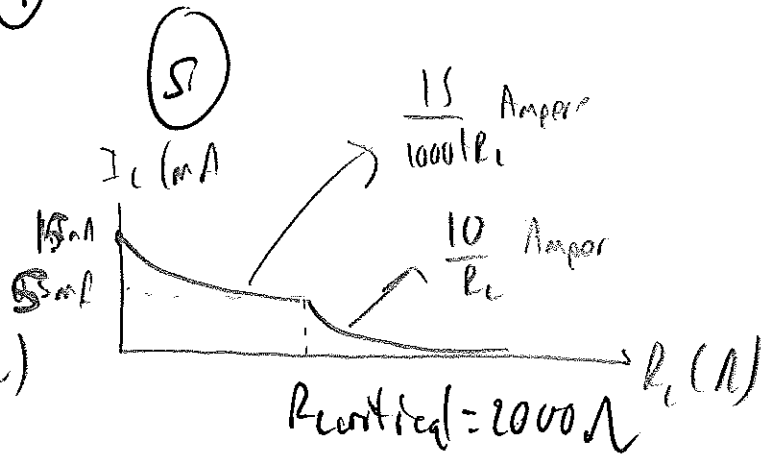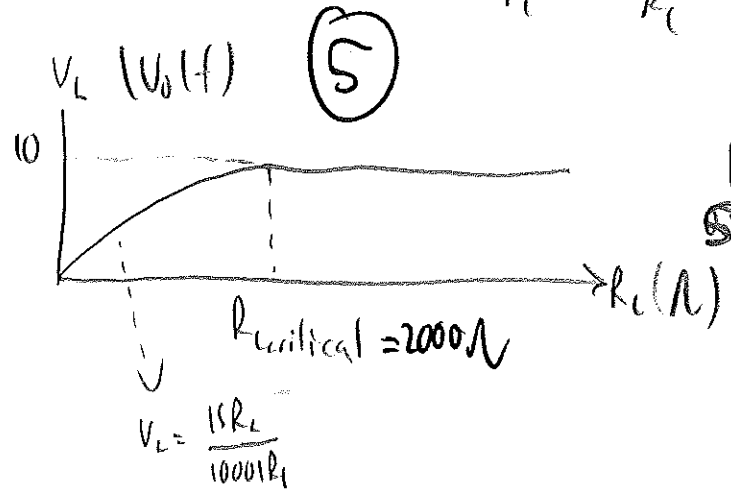$V_L = V_{critical} = 10 \text{ Volt}$ (3)
 $I_L = \frac{V_L}{R_L} = \frac{10}{R_L}$ (4)



Q2

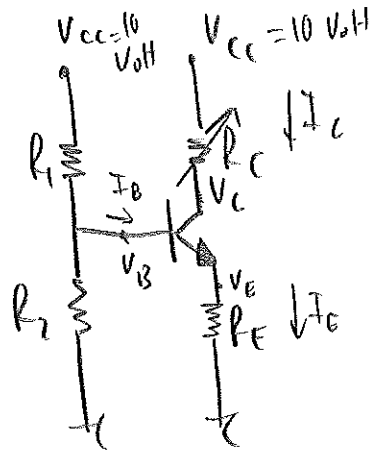

$V_{cc} = 10 \text{ Volt}$
 $\beta = 99$
 $R_E = 100 \Omega$
 $R_1 = R_2 = 10000 \Omega$
 $V_{cc} = 10 \text{ Volt}$
 $V_{BE_{active}} = 0.8$
 $V_{BE_{sat}} = 0.8$
 $V_{CE_{sat}} = 0.8$

$$\frac{V_{cc} - V_B}{R_1} = \frac{V_B}{R_2} + I_B \quad (8)$$

$$I_B = \frac{V_B - V_{BE_{sat}}}{R_E (\beta + 1)} \quad (8)$$

$$\frac{V_{cc} - V_B}{R_1} = \frac{V_B}{R_2} + \frac{V_B - V_{BE_{active}}}{R_E (\beta + 1)} \quad (1)$$

$$\frac{V_{cc}}{R_1} + \frac{V_{BE_{active}}}{R_E (\beta + 1)} = V_B \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_E (\beta + 1)} \right]$$

$$\frac{10}{10000} + \frac{0.8}{10000} = V_B \left[\frac{1}{10000} + \frac{1}{10000} + \frac{1}{10000} \right]$$

$$V_B = \frac{\frac{10.8}{10000}}{\frac{3}{10000}} \Rightarrow V_B = 3.6 \text{ Volt} \quad (1)$$

$$V_E = 2.8 \text{ Volt} \quad (1)$$

$$I_B = \frac{V_B - V_{BE_{active}}}{R_E (\beta + 1)}$$

$$I_B = \frac{3.6 - 0.8}{10000} = \frac{2.8}{10000} = 0.28 \text{ mA} \quad (1)$$

if transistor is in sat region $V_{BE_{sat}} = V_{CE_{sat}}$

$$V_{B_{sat}} = V_{C_{sat}} = 3.6 \text{ Volt} \quad (3 \text{ Question})$$

$$V_C = V_{cc} - R_C I_C \quad (5)$$

$$V_C = 10 - R_C \beta I_B$$

$$V_C = 10 - R_C \times 99 \times 0.28 \times 10^{-3}$$

$$3.6 = 10 - R_C \times 99 \times 0.28 \times 10^{-3}$$

$$6.4 = R_C \times 99 \times 0.28 \times 10^{-3} \quad (2)$$

$$R_C = \frac{6.4}{99 \times 0.28 \times 10^{-3}}$$

$$R_C = \frac{6400}{99 \times 0.28} = R_{C_{max}}$$

Page ?

$$\text{Gain} = - \frac{99}{100} \frac{(R_c || R_L)}{(r_e || R_e)} = - \frac{99}{100} \frac{R_c || R_L}{200} \quad (3)$$

~~Gain = -10 $\frac{99}{20000} R_c || R_L$~~

~~$$\frac{20000}{99} = R_c || R_L$$~~

$$10 \leq \frac{99}{20000} R_c || R_L$$

$$\frac{200000}{99} < R_c || R_L$$

$$2020 \text{ (1000)} < R_c || R_L \quad (1)$$

~~$R_c || R_L > 1000$~~

~~$R_c = 2000 \quad R_L = 2100 \quad R_c || R_L = 1050$~~

if $R_c = R_L$ let $R_c = R_L = 4500 \quad R_c || R_L = 2250$

(1) so c'm